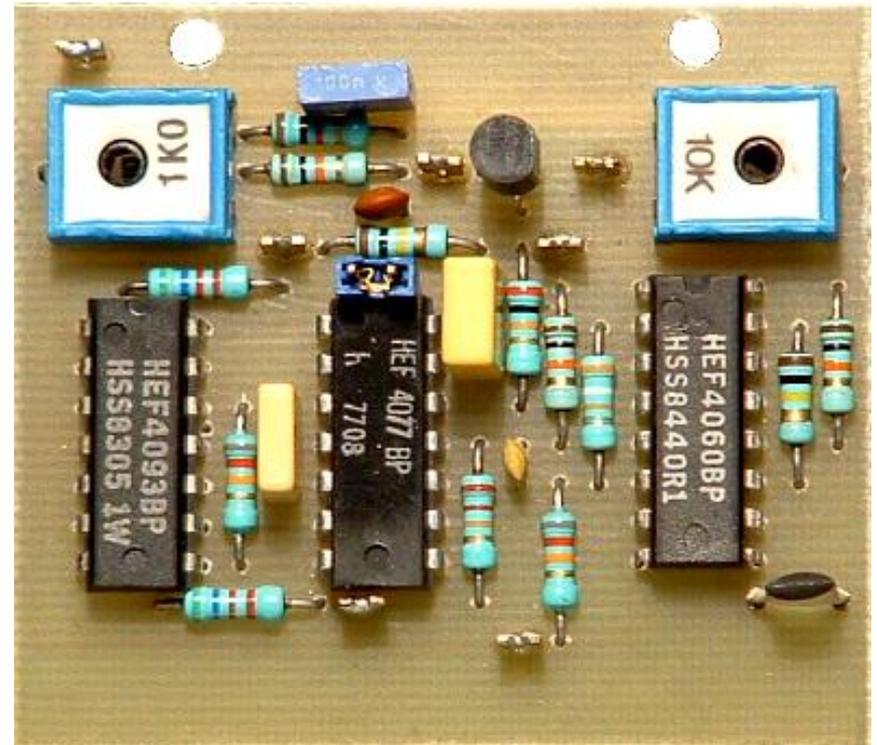



# Chapter 25 : Electric circuits

- Voltage and current
- Series and parallel circuits
- Resistors and capacitors
- Kirchoff's rules for analysing circuits


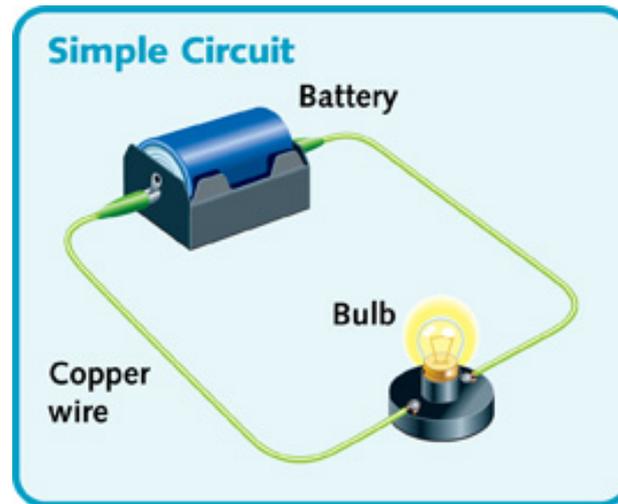
# Electric circuits



- Closed loop of electrical components around which **current** can flow, driven by a **potential difference**



- Current (in Amperes A) is the rate of flow of charge
- Potential difference (in volts V) is the work done on charge
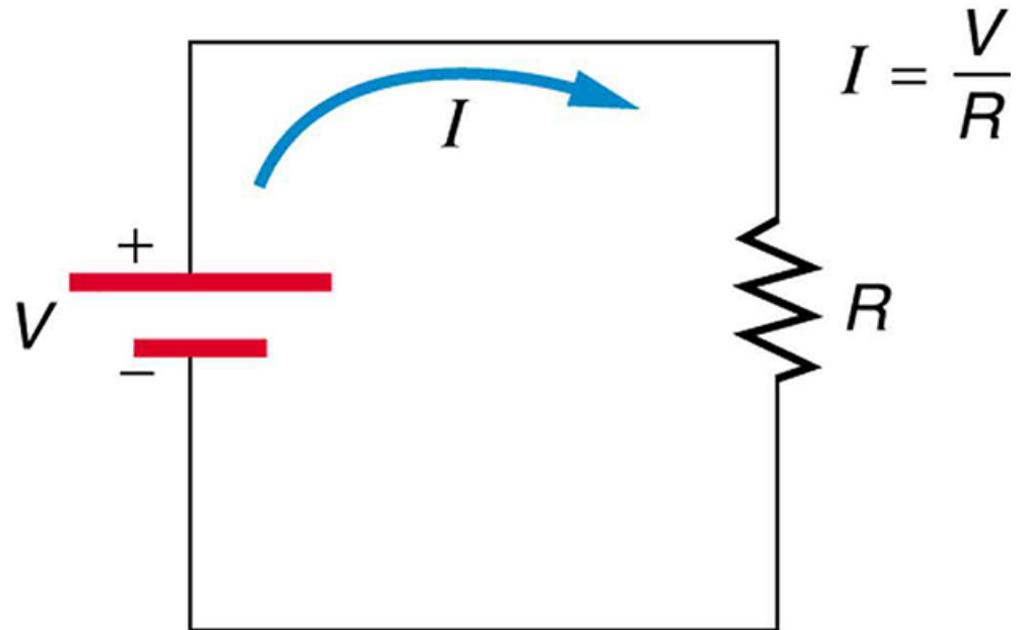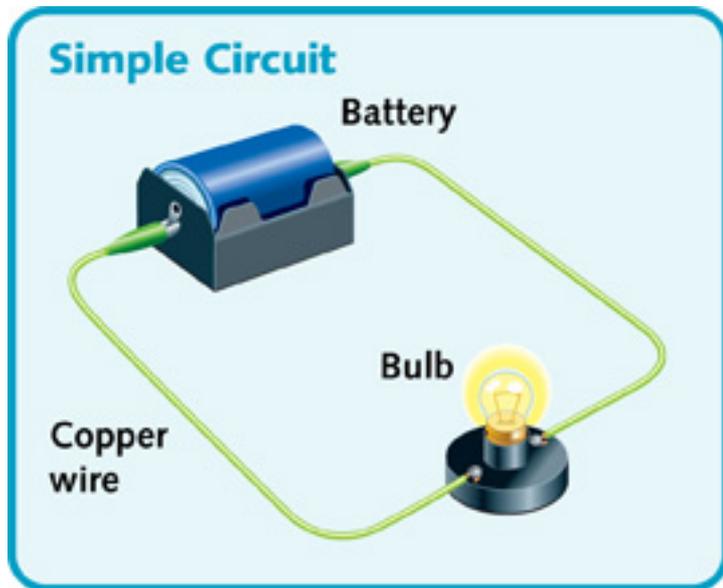
# Electric circuits


- May be represented by a **circuit diagram**.  
Here is a simple case:



- R is the resistance (in Ohms  $\Omega$ ) to current flow

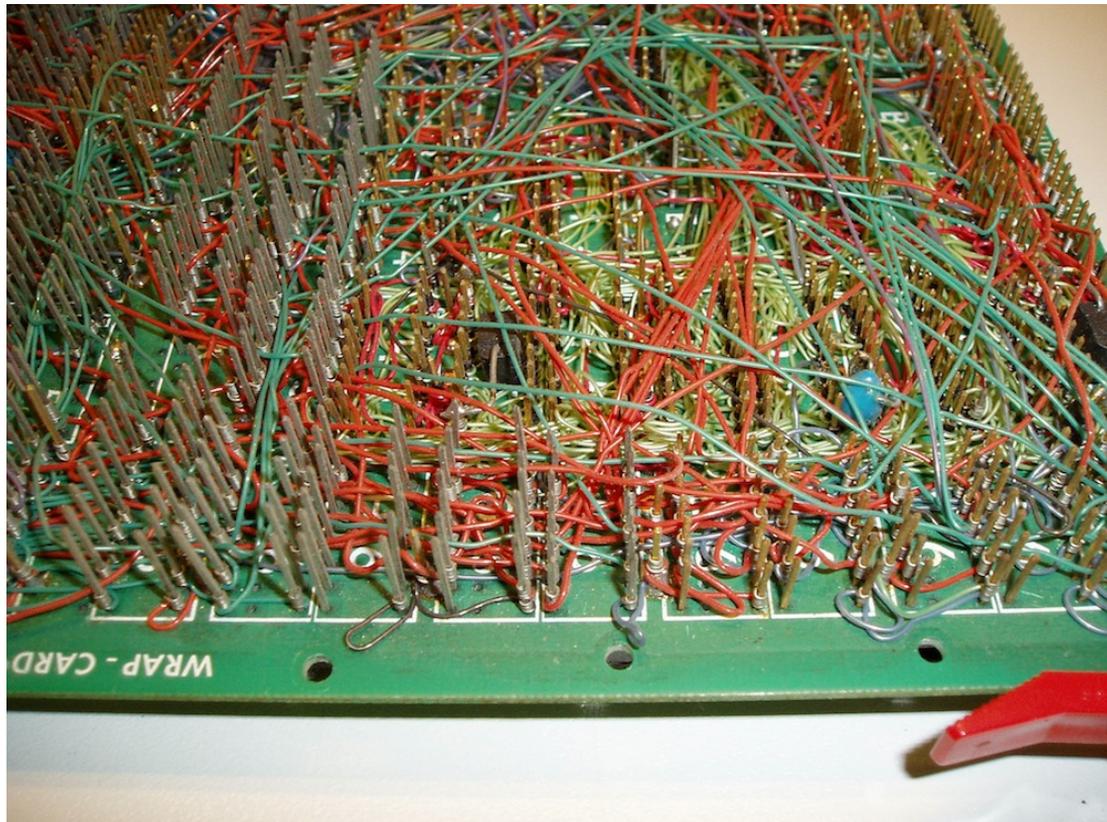
# Electric circuits

- Same principles apply in more complicated cases!




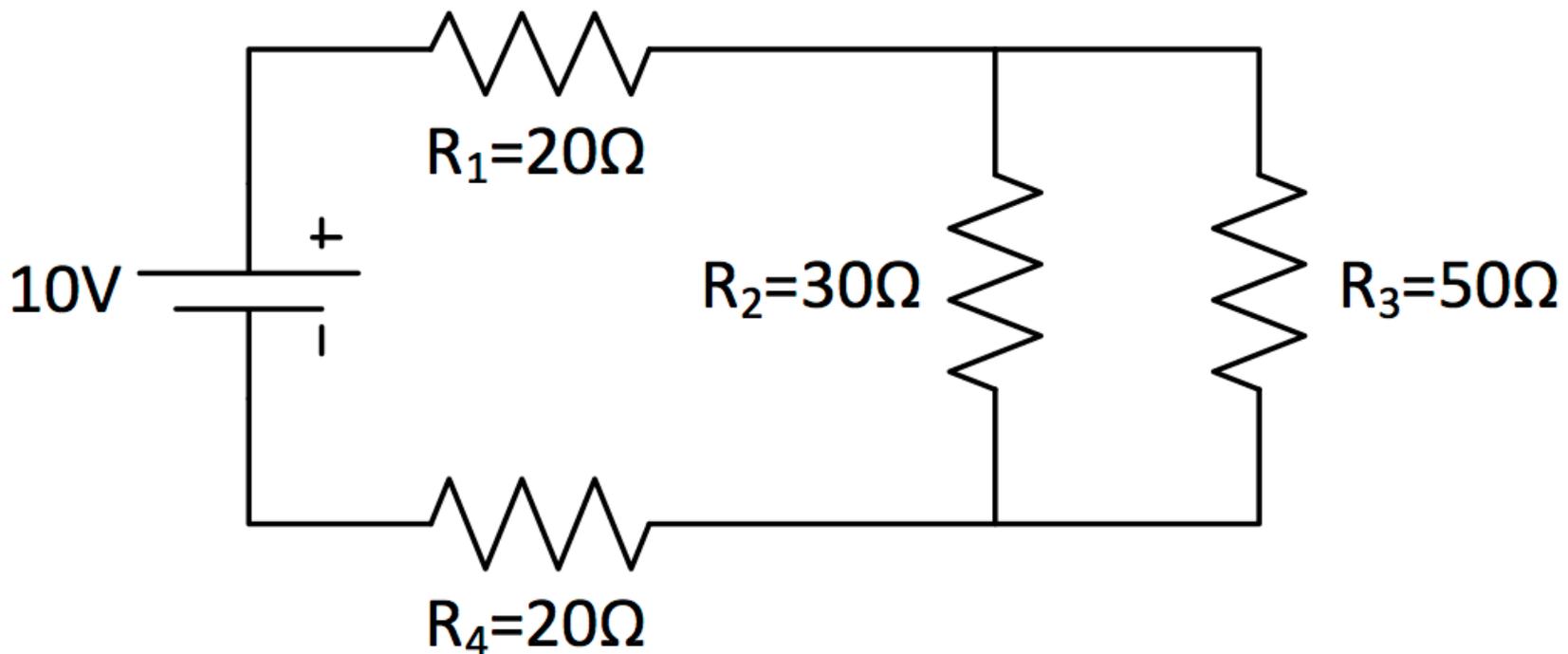
# Electric circuits

- How do we deal with a more complicated case?  
What is the current flowing from the battery?


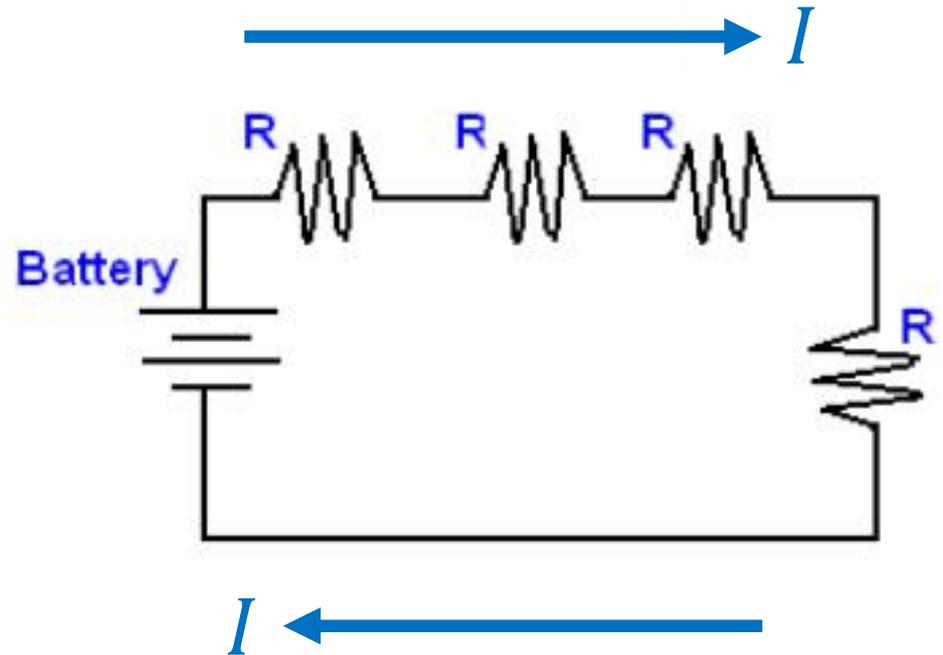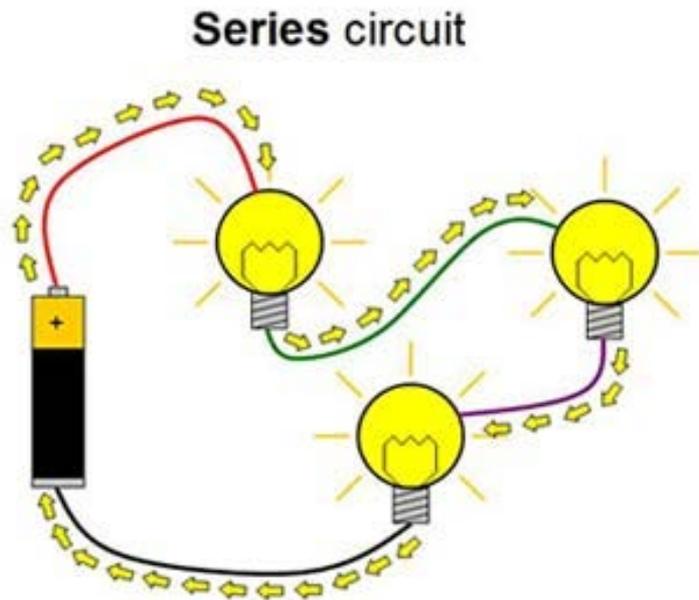
# Electric circuits

- When components are connected **in series**, the **same electric current** flows through them





- Charge conservation : current cannot disappear!

# Electric circuits

- When components are connected **in parallel**, the **same potential difference** drops across them


Parallel circuit

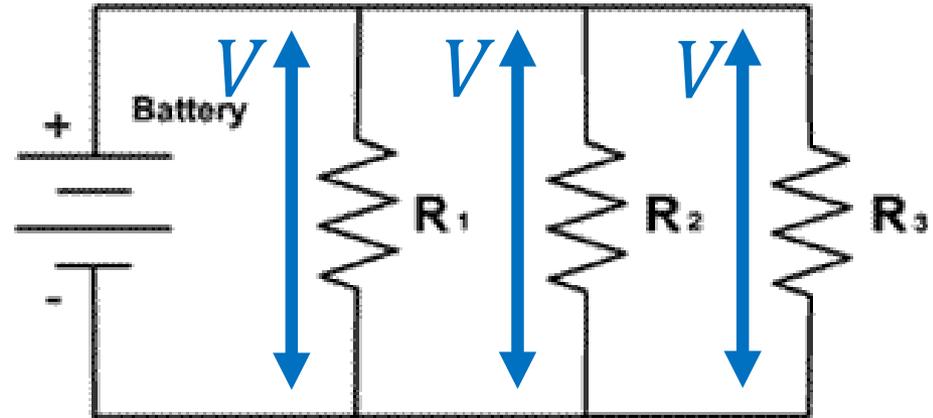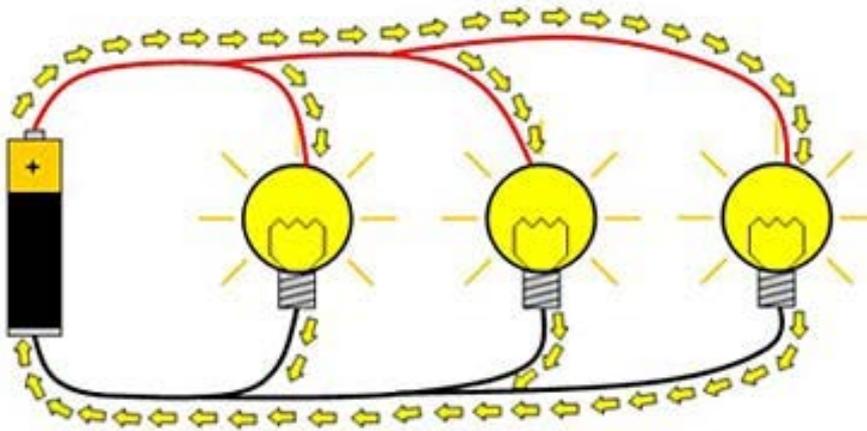

- Points connected by a wire are at the same voltage!

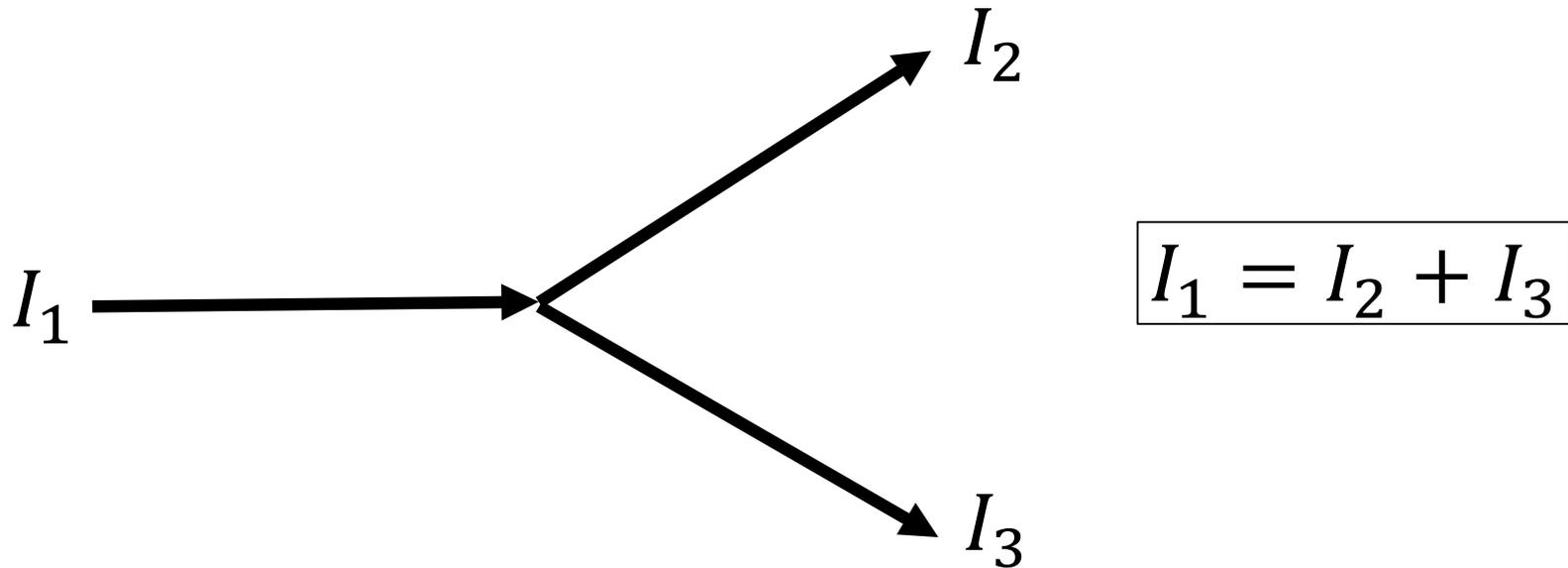
# Electric circuits

- When there is a junction in the circuit, the inward and outward currents to the junction are the same




- Charge conservation : current cannot disappear!

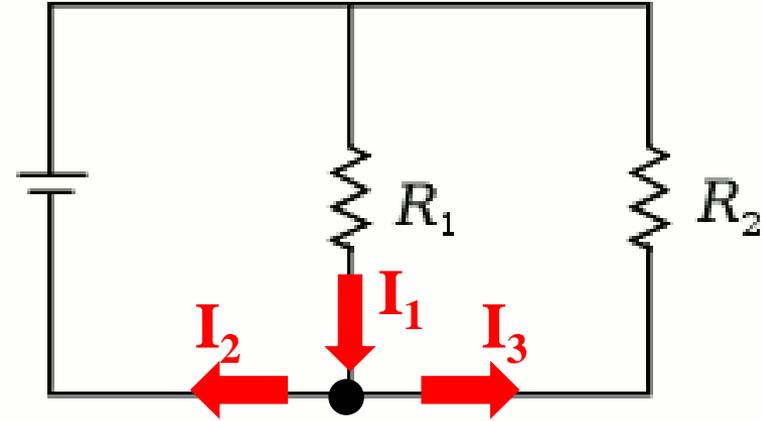
Consider the currents  $I_1$ ,  $I_2$  and  $I_3$  as indicated on the circuit diagram. If  $I_1 = 2.5$  A and  $I_2 = 4$  A, what is the value of  $I_3$ ?



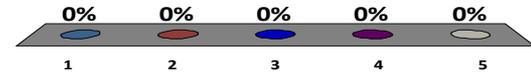1. 6.5 A
2. 1.5 A
3. -1.5 A
4. 0 A
5. The situation is not possible



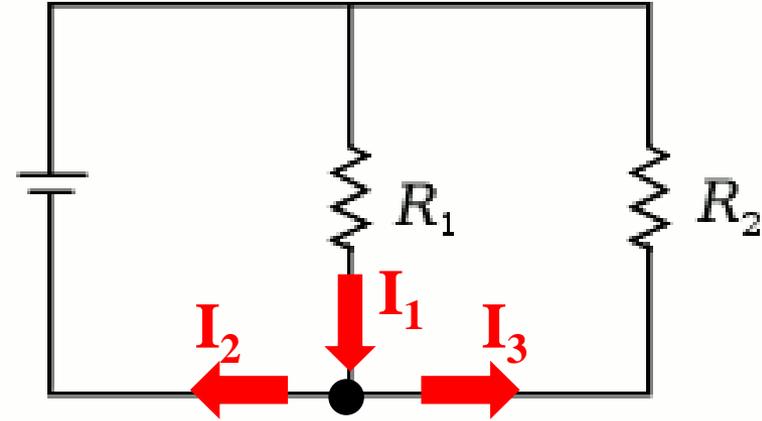Consider the currents  $I_1$ ,  $I_2$  and  $I_3$  as indicated on the circuit diagram. If  $I_1 = 2.5$  A and  $I_2 = 4$  A, what is the value of  $I_3$ ?



current in = current out


$$I_1 = I_2 + I_3$$

$$I_3 = I_1 - I_2$$


$$I_3 = 2.5 - 4 = -1.5 \text{ A}$$

(Negative sign means opposite direction to arrow.)

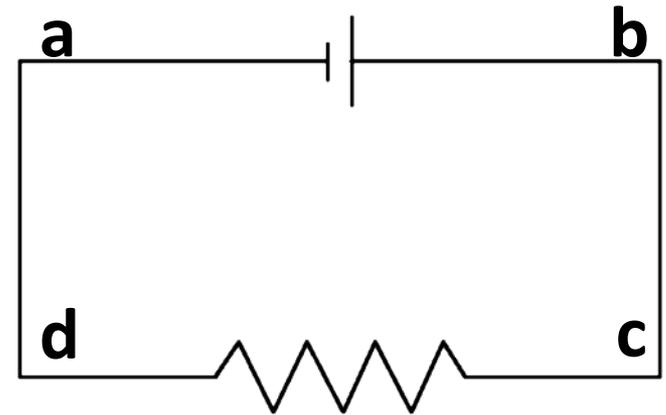A 9.0 V battery is connected to a 3  $\Omega$  resistor. Which is the **incorrect** statement about potential differences (voltages)?




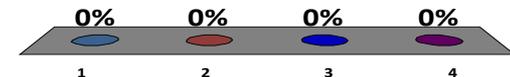1.  $V_b - V_a = 9.0 \text{ V}$
2.  $V_b - V_c = 0 \text{ V}$
3.  $V_c - V_d = 9.0 \text{ V}$
4.  $V_d - V_a = 9.0 \text{ V}$


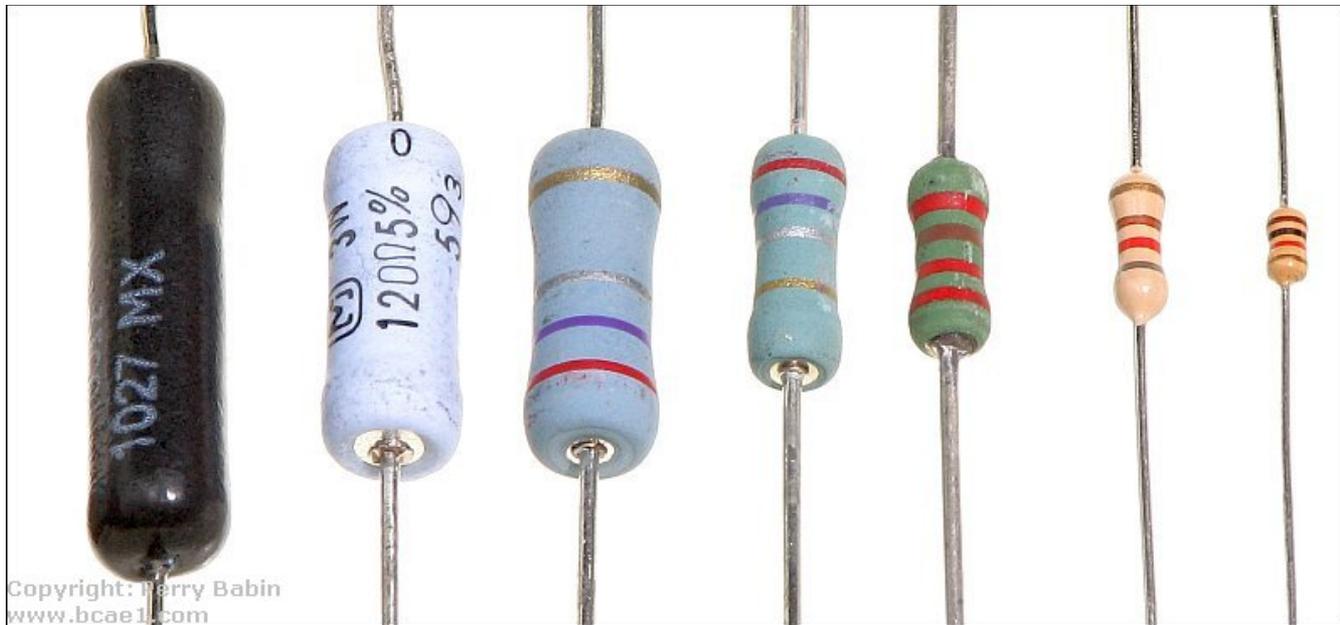
# Resistors in circuits

- **Resistors** are the basic components of a circuit that determine current flow : **Ohm's law**  $I = V/R$



# Resistors in series/parallel

- If two resistors are connected in series, what is the total resistance?



same current  $\longrightarrow I$

$\longrightarrow I$


Potential drop  $V_1 = I R_1$

Potential drop  $V_2 = I R_2$

Total potential drop  $V = V_1 + V_2 = I R_1 + I R_2 = I (R_1 + R_2)$
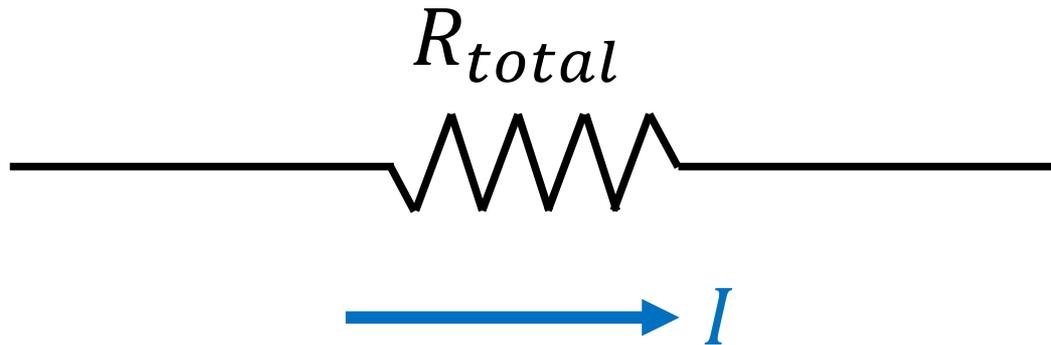
# Resistors in series/parallel

- If two resistors are connected in series, what is the total resistance?



Potential drop  $V = I R_{total} = I (R_1 + R_2)$

$$R_{total} = R_1 + R_2$$

- Total resistance increases in series!


# Resistors in series/parallel

- Total resistance increases in series!



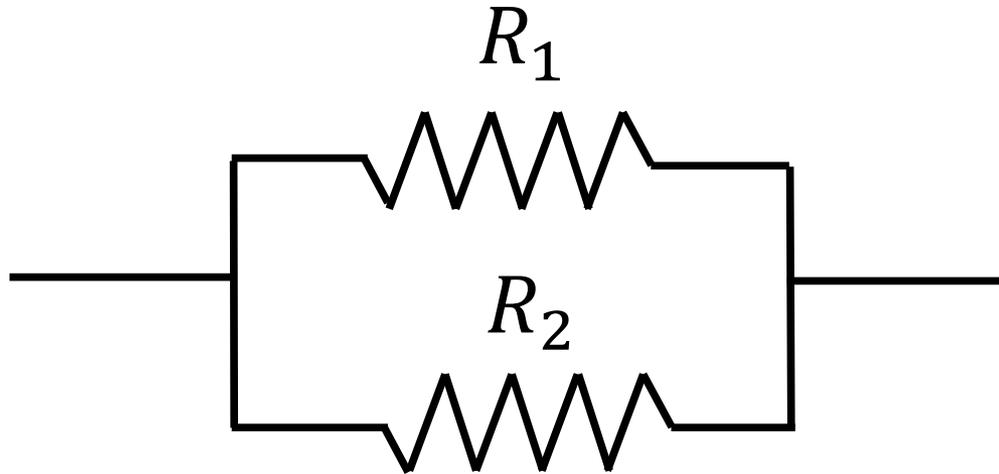
# Resistors in series/parallel

- If two resistors are connected in parallel, what is the total resistance?


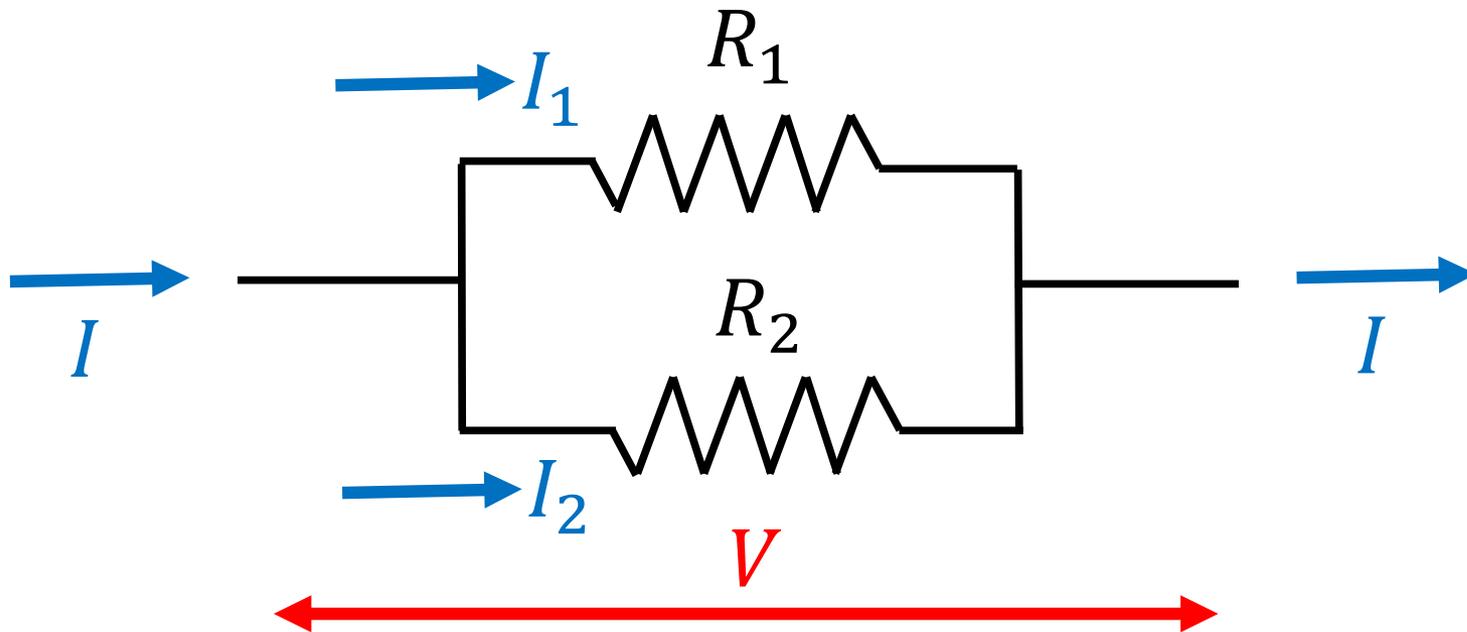
# Resistors in series/parallel


- If two resistors are connected in parallel, what is the total resistance?



$$\text{Total current } I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$
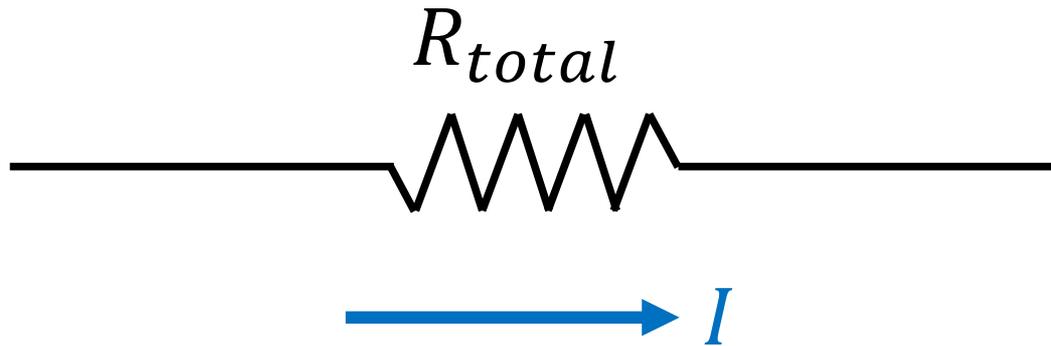
# Resistors in series/parallel

- If two resistors are connected in parallel, what is the total resistance?



$$\text{Current } I = \frac{V}{R_{total}} = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2}$$

- Total resistance decreases in parallel!


# Resistors in series/parallel

- Total resistance decreases in parallel!



# Resistors in series/parallel

- What's the current flowing?

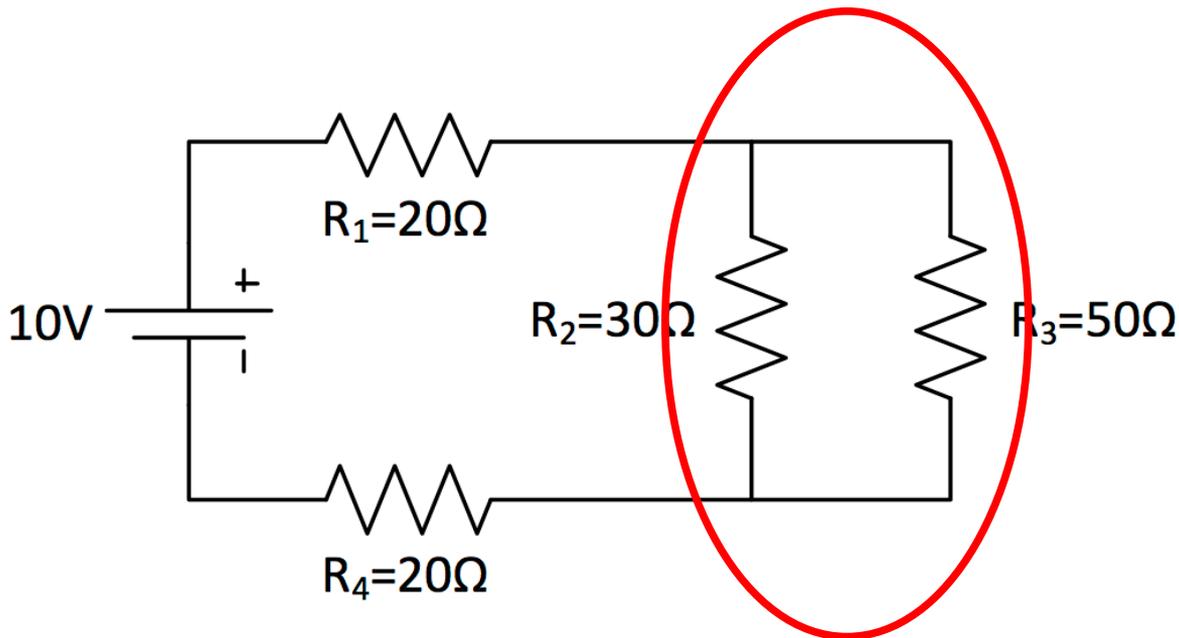

(1) Combine these 2 resistors in parallel:

$$\frac{1}{R_{pair}} = \frac{1}{30} + \frac{1}{50}$$

$$R_{pair} = 18.75 \Omega$$



(2) Combine all the resistors in series:

$$R_{total} = 20 + 18.75 + 20 = 58.75 \Omega$$

$$(3) \text{ Current } I = \frac{V}{R_{total}} = \frac{10}{58.75} = 0.17 \text{ A}$$

If an additional resistor,  $R_2$ , is added in series to the circuit, what happens to the **power dissipated** by  $R_1$ ?

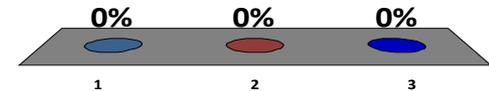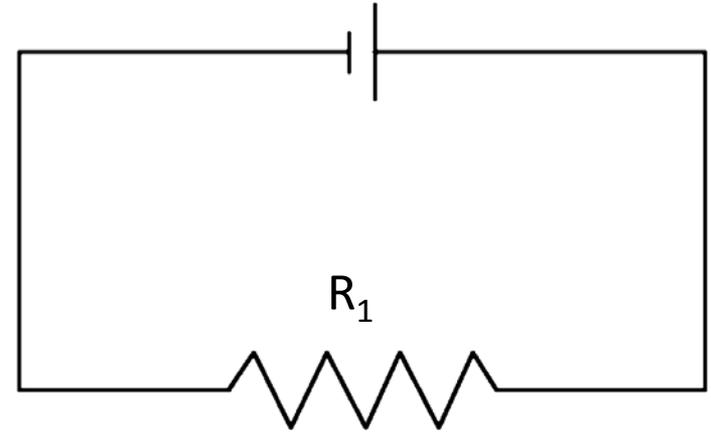
1. **Increases**
2. **Decreases**
3. **Stays the same**




$$V = IR$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

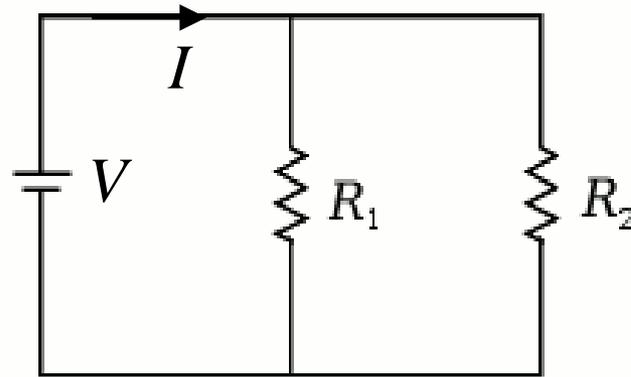If an additional resistor,  $R_3$ , is added in parallel to the circuit, what happens to the **total current, I**?




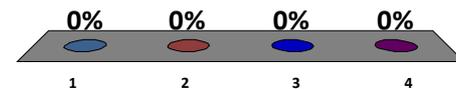
1. Increases
2. Decreases
3. Stays the same
4. Depends on R values



Parallel resistors: reciprocal effective resistance is sum of reciprocal resistances

$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

# Series vs. Parallel

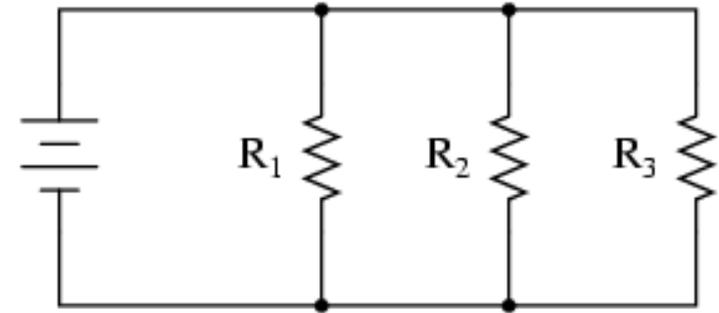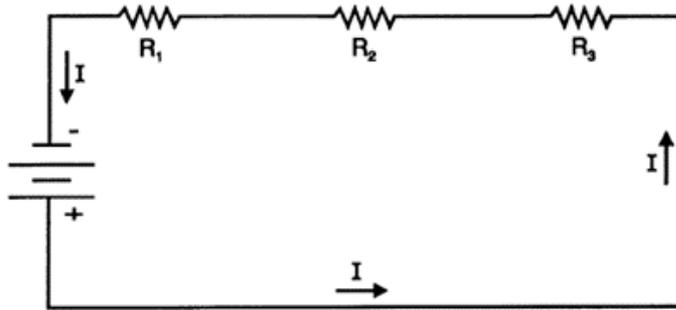

## CURRENT

Same current through all series elements

Current “splits up” through parallel branches

## VOLTAGE

Voltages add to total circuit voltage

Same voltage across all parallel branches

## RESISTANCE


Adding resistance increases total  $R$

Adding resistance reduces total  $R$

String of Christmas lights – connected in *series*  
Power outlets in house – connected in *parallel*
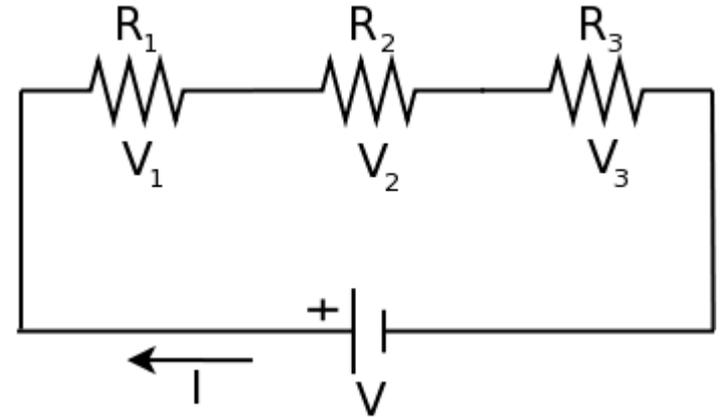
# Voltage divider

Consider a circuit with several resistors in series with a battery.



Current in circuit: 
$$I = \frac{V}{R_{total}} = \frac{V}{R_1 + R_2 + R_3}$$

The potential difference across one of the resistors (e.g.  $R_1$ )

$$V_1 = IR_1 = V \frac{R_1}{R_1 + R_2 + R_3}$$

The fraction of the total voltage that appears across a resistor in series is the ratio of the given resistance to the total resistance.



What must be the resistance  $R_1$  so that  $V_1 = 2.0 \text{ V}$ ?

1.  $0.80 \Omega$

2.  $1.2 \Omega$

3.  $6.0 \Omega$


4.  $30 \Omega$

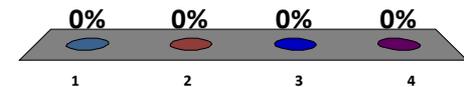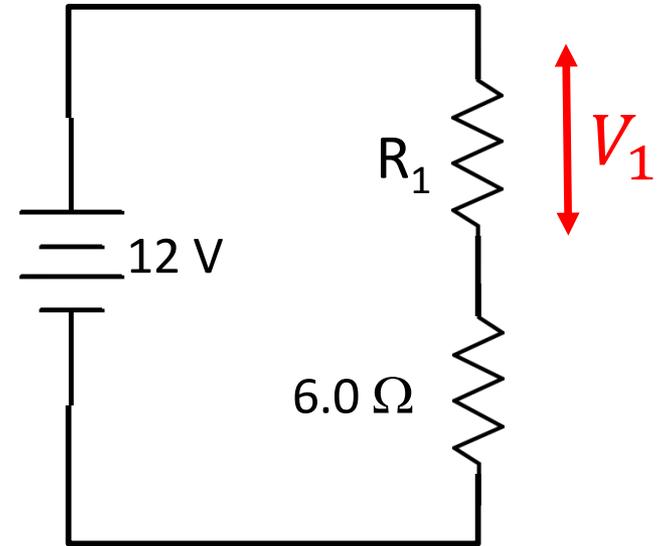

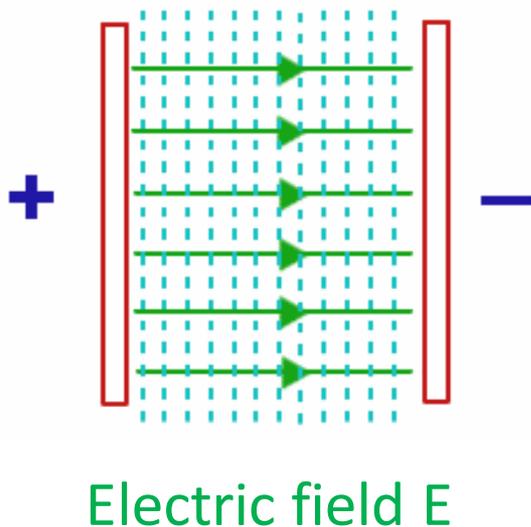
# Capacitors

- A **capacitor** is a device in a circuit which **can be used to store charge**

A capacitor consists of two charged plates ...



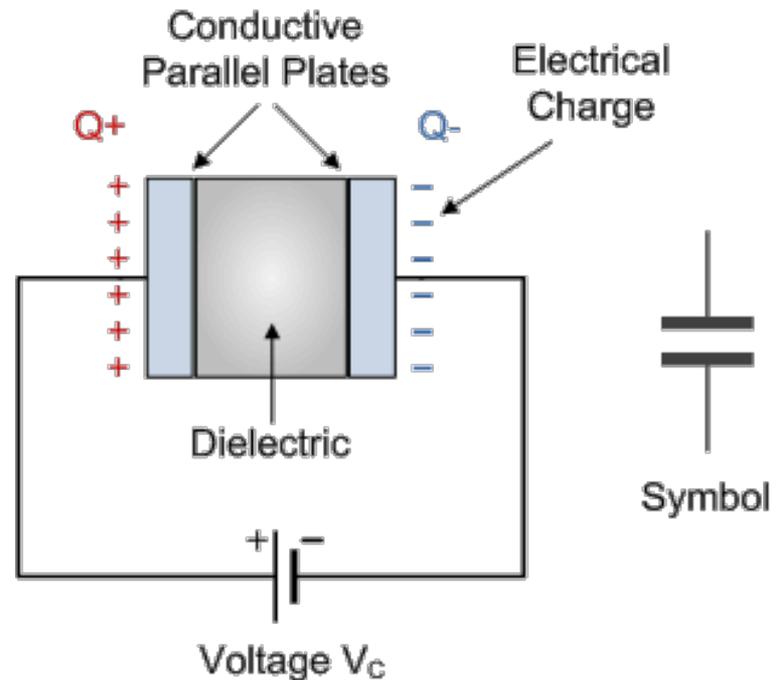It's charged by connecting it to a battery ...



# Capacitors


- A **capacitor** is a device in a circuit which **can be used to store charge**

Example : store and release energy ...


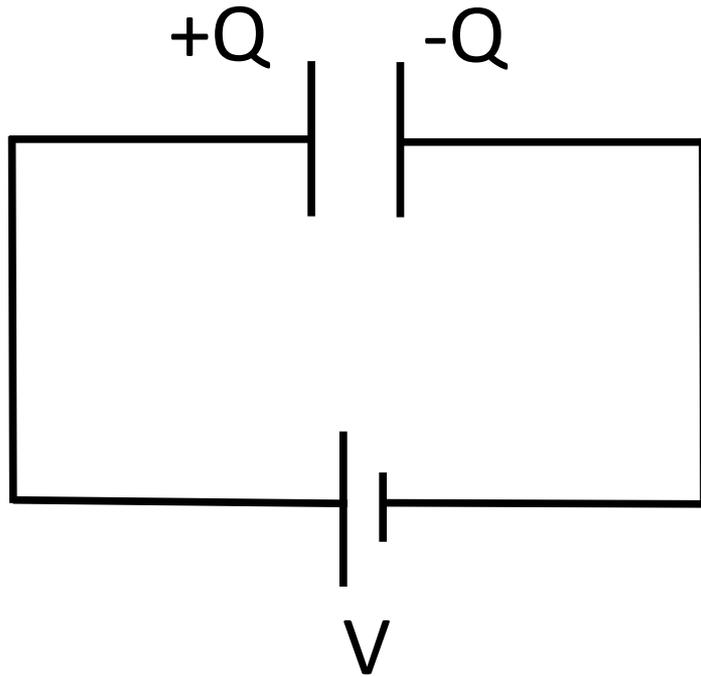
# Capacitors

- The **capacitance C** measures the amount of charge  $Q$  which can be stored for given potential difference  $V$



$$C = \frac{Q}{V}$$

$$Q = C V$$


(Value of  $C$  depends on geometry...)

- Unit of capacitance is **Farads [F]**


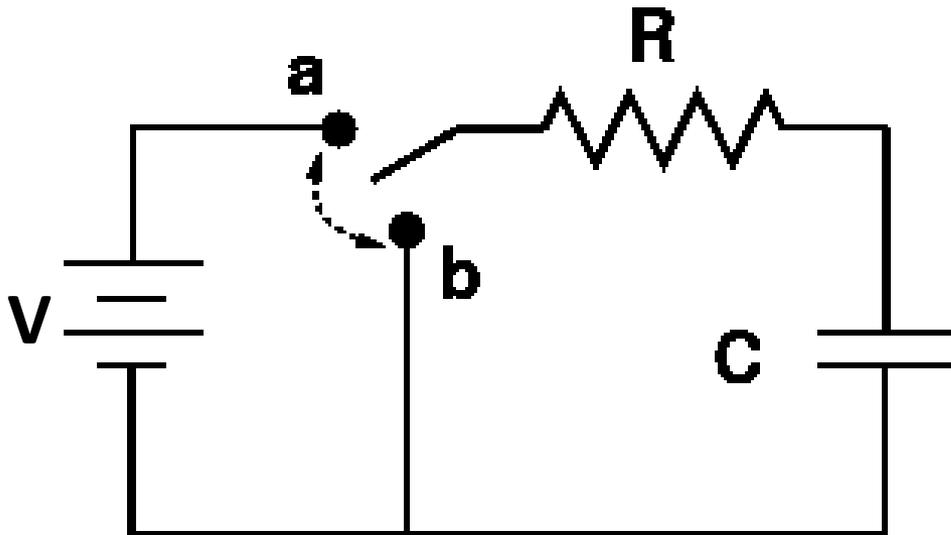
# Resistor-capacitor circuit


- Consider the following circuit with a resistor and a capacitor in series



What happens when we connect the circuit?
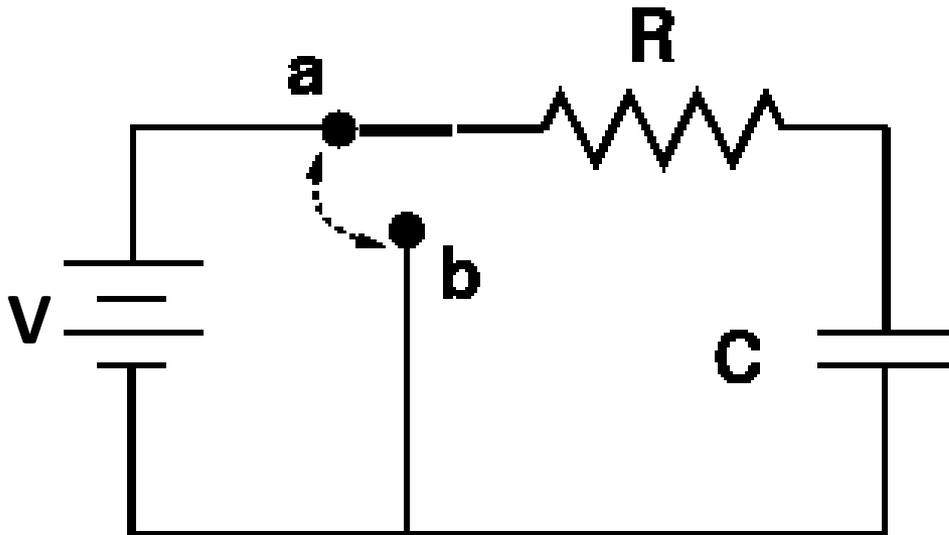
# Resistor-capacitor circuit



- When the switch is connected, the battery charges up the capacitor



- Move the switch to point  $a$
- Initial current flow  $I=V/R$
- Charge  $Q$  flows from battery onto the capacitor
- Potential across the capacitor  $V_C=Q/C$  increases
- Potential across the resistor  $V_R$  decreases
- Current decreases to zero

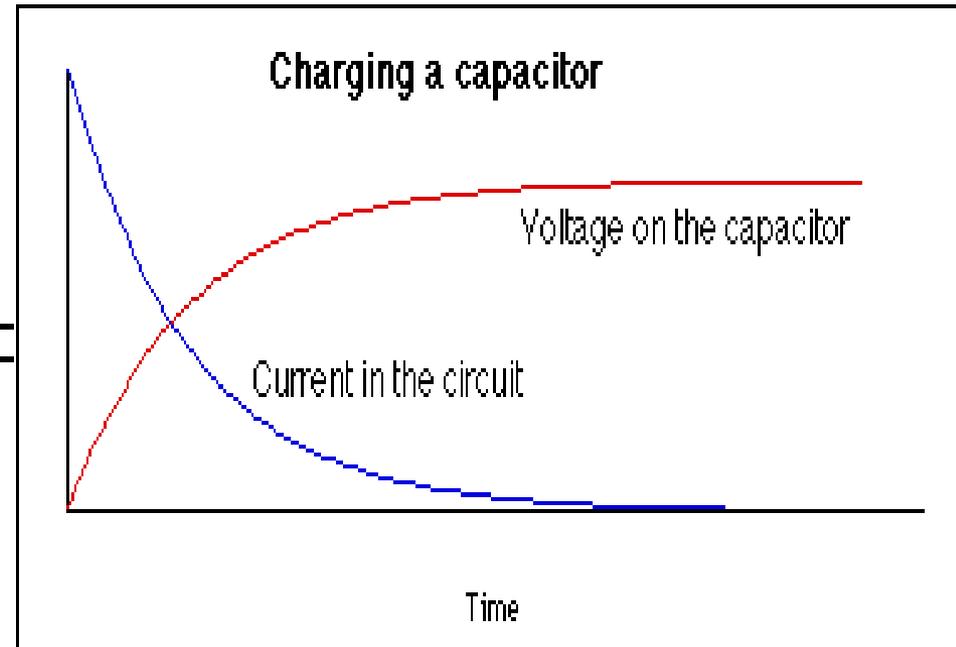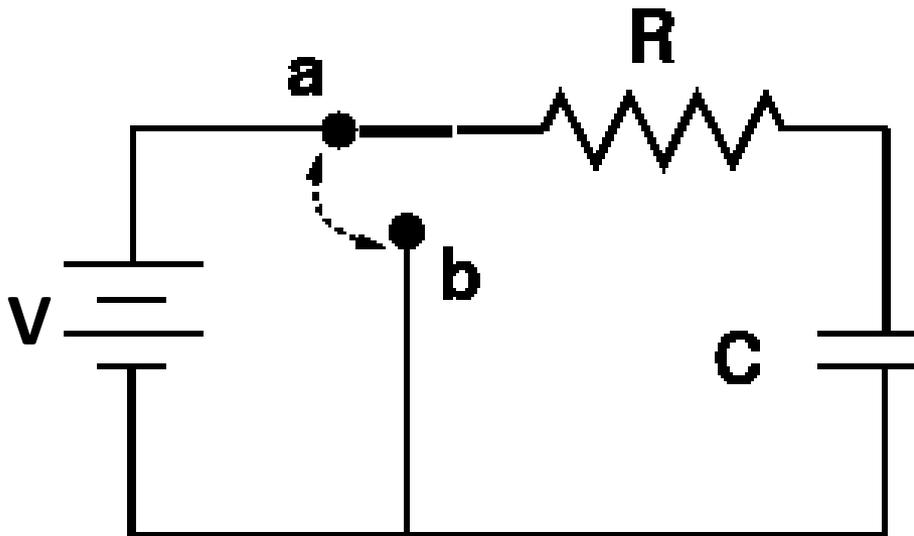
# Resistor-capacitor circuit

- When the switch is connected, the battery charges up the capacitor


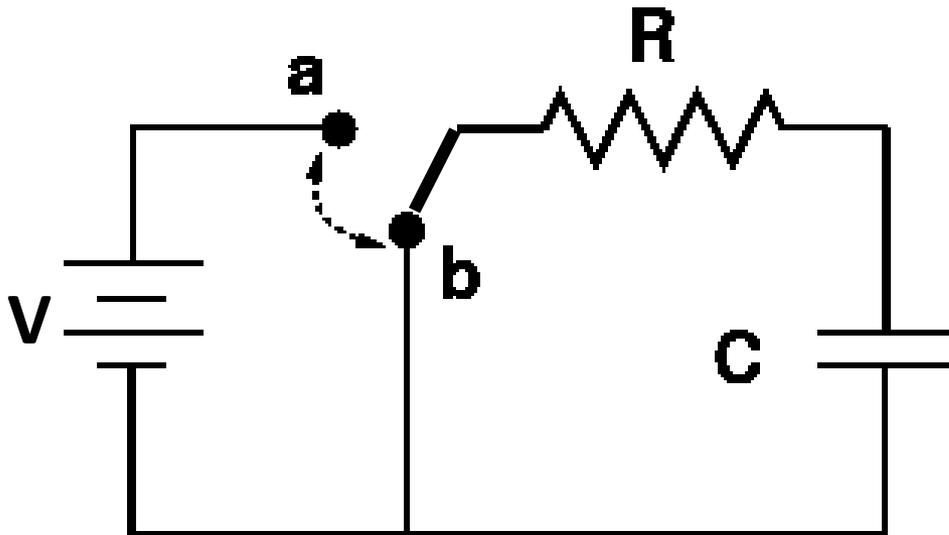
# Resistor-capacitor circuit



- When the battery is disconnected, the capacitor pushes charge around the circuit



- Move the switch to point b
- Initial current flow  $I = V_C / R$
- Charge flows from one plate of capacitor to other
- Potential across the capacitor  $V_C = Q / C$  decreases
- Current decreases to zero

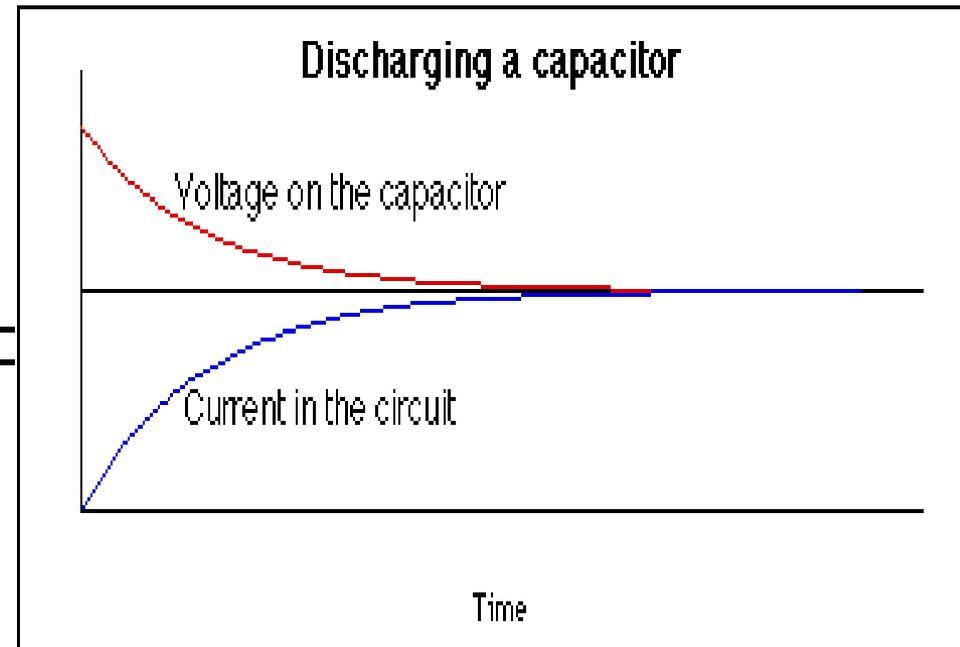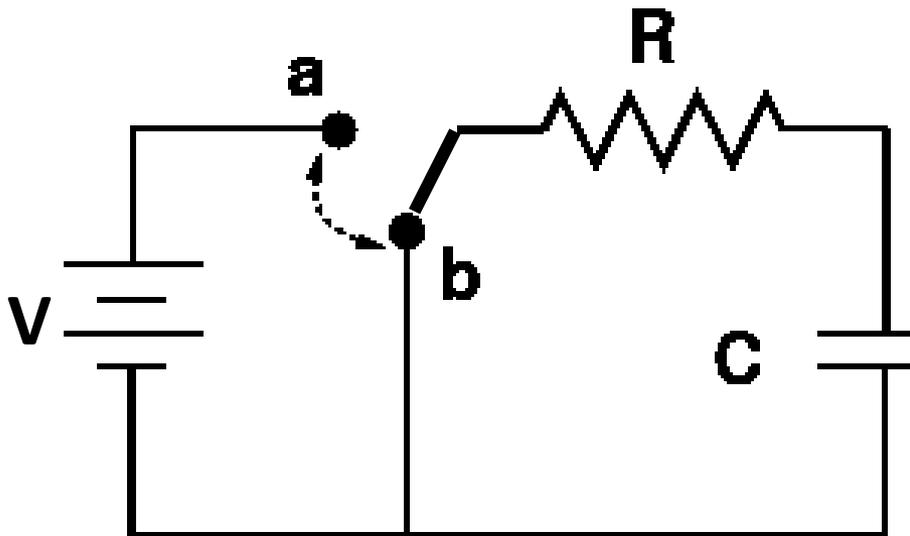
# Resistor-capacitor circuit

- When the battery is disconnected, the capacitor pushes charge around the circuit


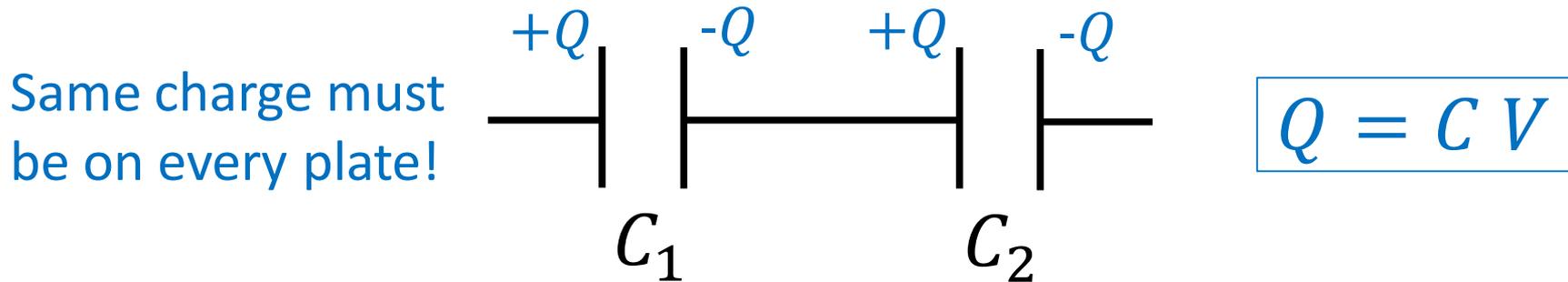
# Capacitors in series/parallel

- If two capacitors are connected in series, what is the total capacitance?




$$\text{Potential drop } V_1 = Q/C_1 \quad \text{Potential drop } V_2 = Q/C_2$$

$$\text{Total potential drop } V = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2} = Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$
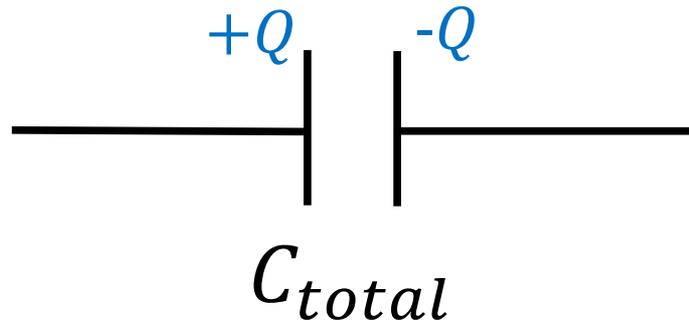
# Capacitors in series/parallel

- If two capacitors are connected in series, what is the total capacitance?



$$Q = C V$$


$$\text{Potential drop } V = \frac{Q}{C_{total}} = Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$

- Total capacitance decreases in series!
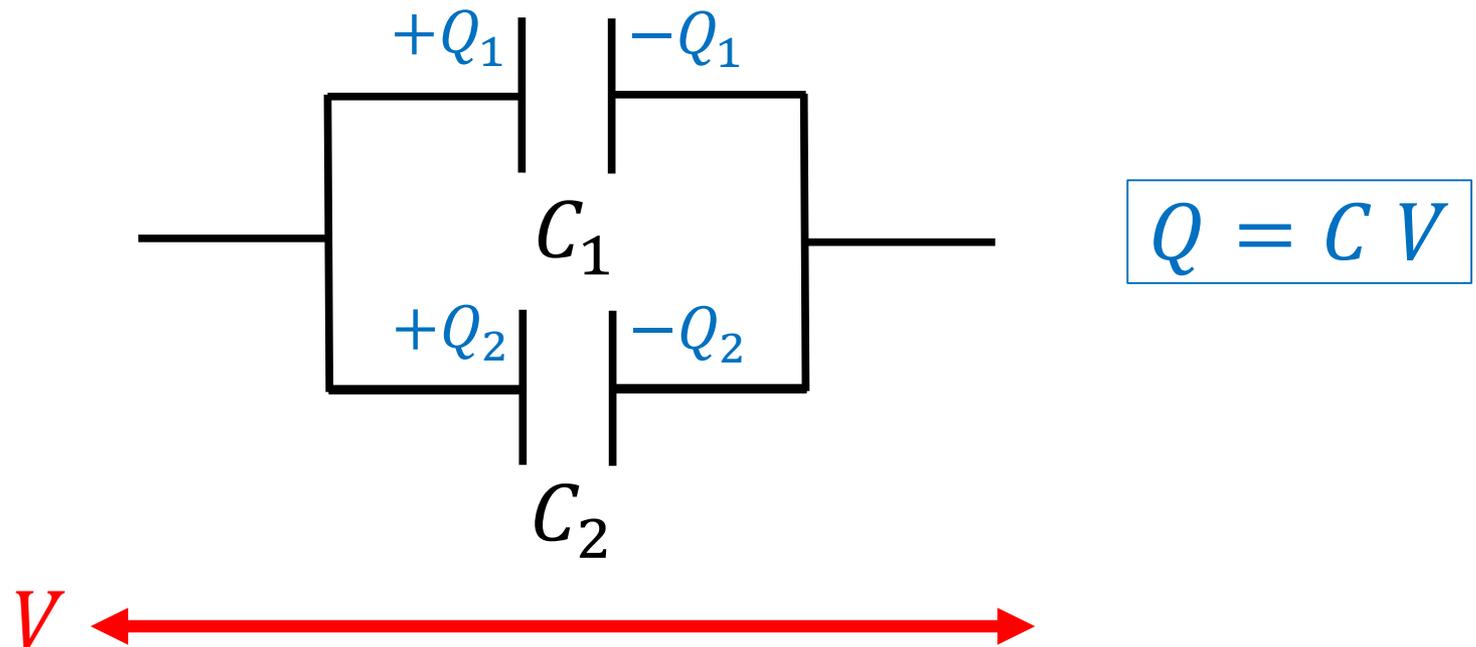
# Capacitors in series/parallel


- If two capacitors are connected in parallel, what is the total capacitance?



$$\text{Total charge } Q = Q_1 + Q_2 = C_1 V + C_2 V = (C_1 + C_2) V$$
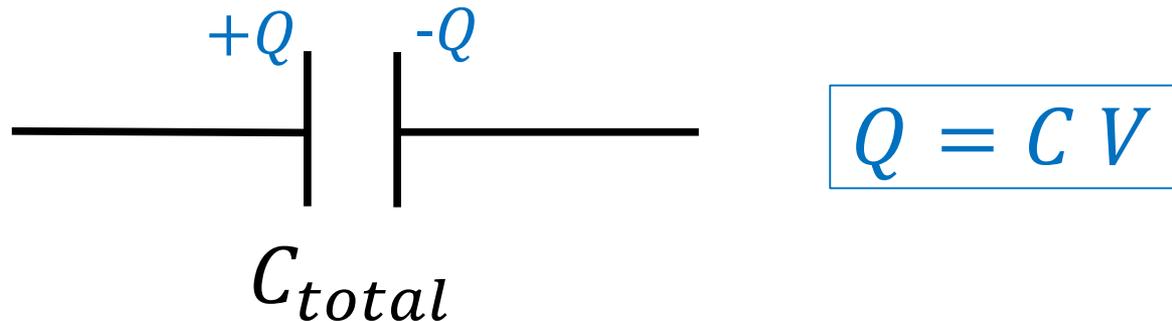
# Capacitors in series/parallel

- If two capacitors are connected in parallel, what is the total capacitance?




Total charge  $Q = C_{total}V = (C_1 + C_2)V$


$$C_{total} = C_1 + C_2$$

- Total capacitance increases in parallel!

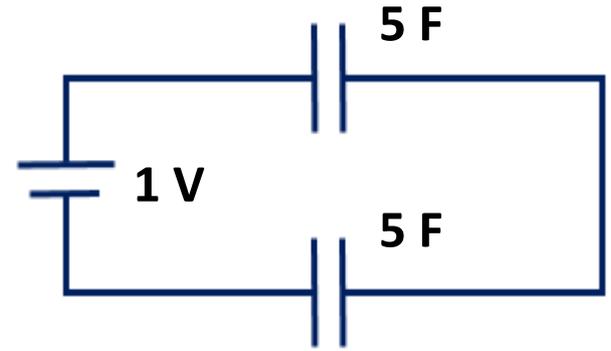Two 5.0 F capacitors are in series with each other and a 1.0 V battery. Calculate the charge on each capacitor ( $Q$ ) and the total charge drawn from the battery ( $Q_{\text{total}}$ ).



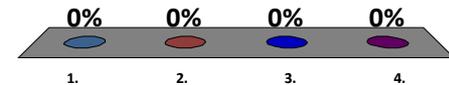
1.  $Q = 5.0 \text{ C}, Q_{\text{total}} = 5.0 \text{ C}$
2.  $Q = 0.25 \text{ C}, Q_{\text{total}} = 0.50 \text{ C}$
3.  $Q = 2.5 \text{ C}, Q_{\text{total}} = 2.5 \text{ C}$
4.  $Q = 2.5 \text{ C}, Q_{\text{total}} = 5.0 \text{ C}$



$$Q = CV$$

$$\frac{1}{C_{\text{total}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

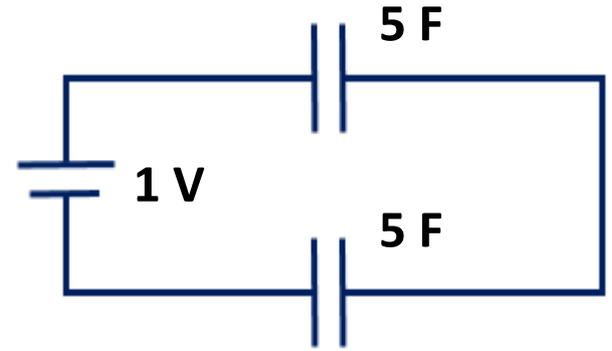Two 5.0 F capacitors are in series with each other and a 1.0 V battery. Calculate the charge on each capacitor ( $Q$ ) and the total charge drawn from the battery ( $Q_{\text{total}}$ ).




Potential difference across each capacitor = 0.5 V

Charge on each capacitor  $Q = CV = 5 \times 0.5 = 2.5 C$


$$\frac{1}{C_{\text{total}}} = \frac{1}{C_1} + \frac{1}{C_2} \rightarrow \frac{1}{C_{\text{total}}} = \frac{1}{5} + \frac{1}{5} = \frac{2}{5} \rightarrow C_{\text{total}} = 2.5 F$$

$$Q_{\text{total}} = C_{\text{total}} V = 2.5 \times 1 = 2.5 C$$

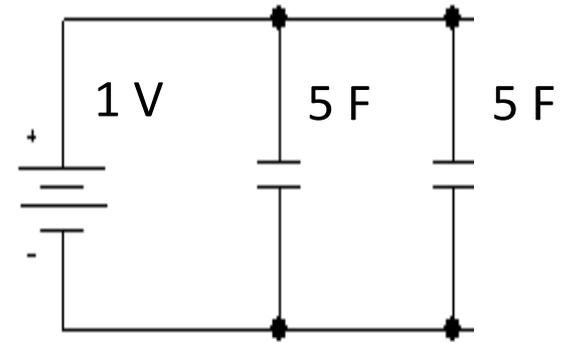Two 5.0 F capacitors are in parallel with each other and a 1.0 V battery. Calculate the charge on each capacitor ( $Q$ ) and the total charge drawn from the battery ( $Q_{\text{total}}$ ).



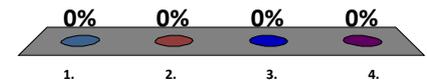
1.  $Q = 5.0 \text{ C}$ ,  $Q_{\text{total}} = 5.0 \text{ C}$
2.  $Q = 0.2 \text{ C}$ ,  $Q_{\text{total}} = 0.4 \text{ C}$
3.  $Q = 5.0 \text{ C}$ ,  $Q_{\text{total}} = 10 \text{ C}$
4.  $Q = 2.5 \text{ C}$ ,  $Q_{\text{total}} = 2.5 \text{ C}$



$$Q = CV$$

$$C_{\text{total}} = C_1 + C_2 + C_3 + \dots$$

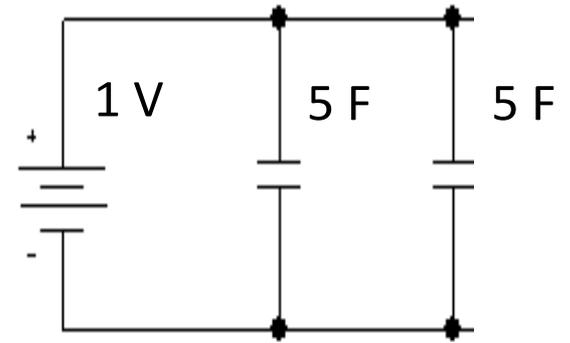Two 5.0 F capacitors are in parallel with each other and a 1.0 V battery. Calculate the charge on each capacitor ( $Q$ ) and the total charge drawn from the battery ( $Q_{\text{total}}$ ).




Potential difference across each capacitor = 1 V


Charge on each capacitor  $Q = CV = 5 \times 1 = 5 C$

$$Q_{\text{total}} = 10 C$$

# Resistors vs. Capacitors

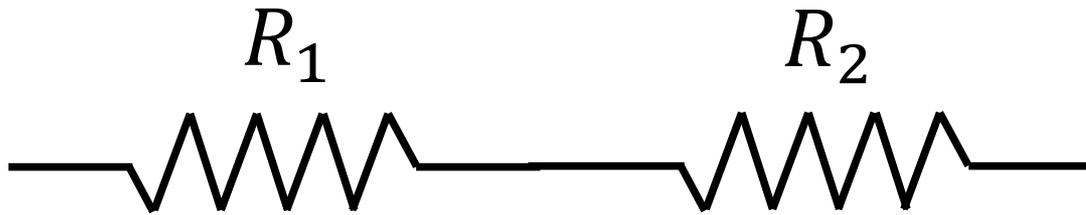


$$R_{total} = R_1 + R_2$$

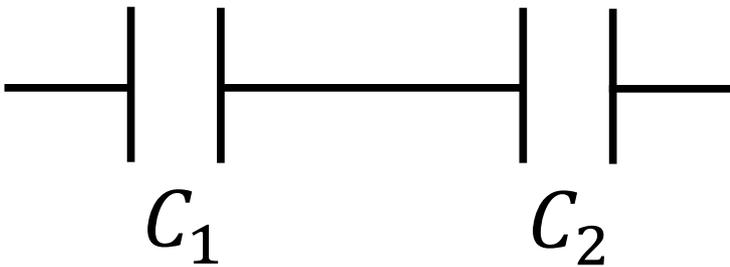


$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$

# Resistors vs. Capacitors

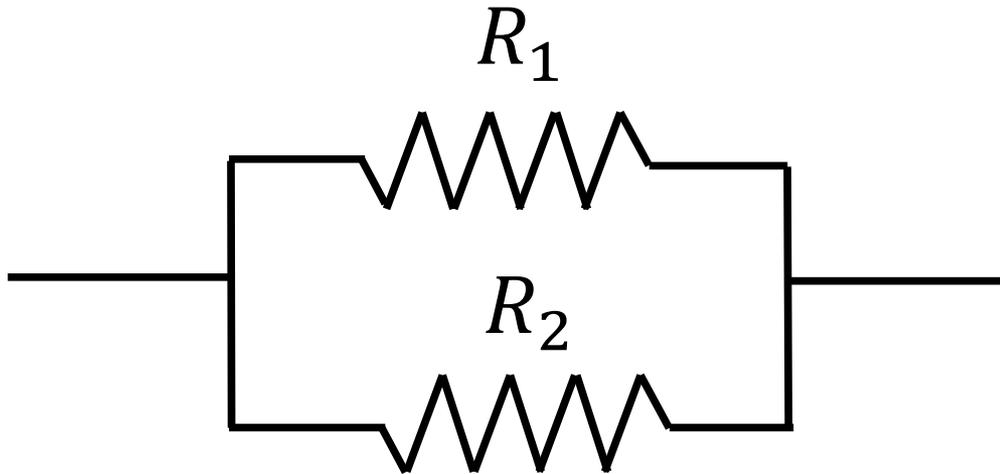

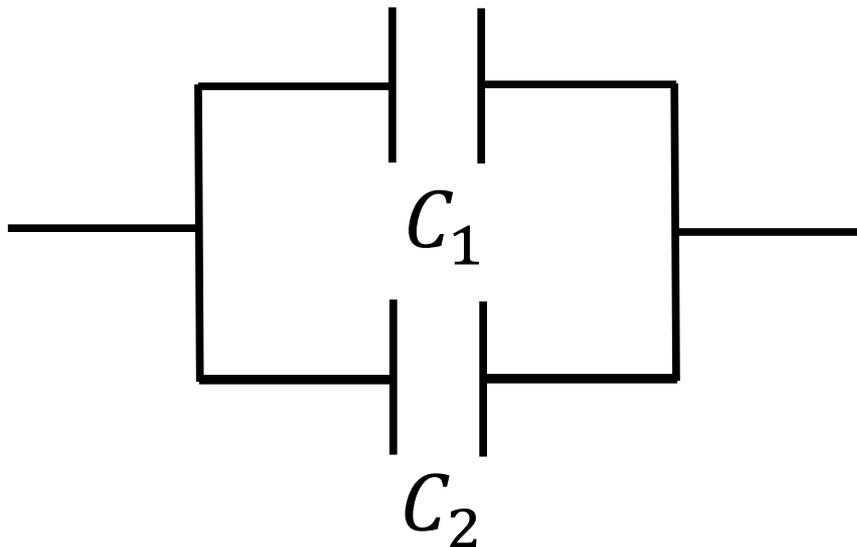
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$C_{total} = C_1 + C_2$$
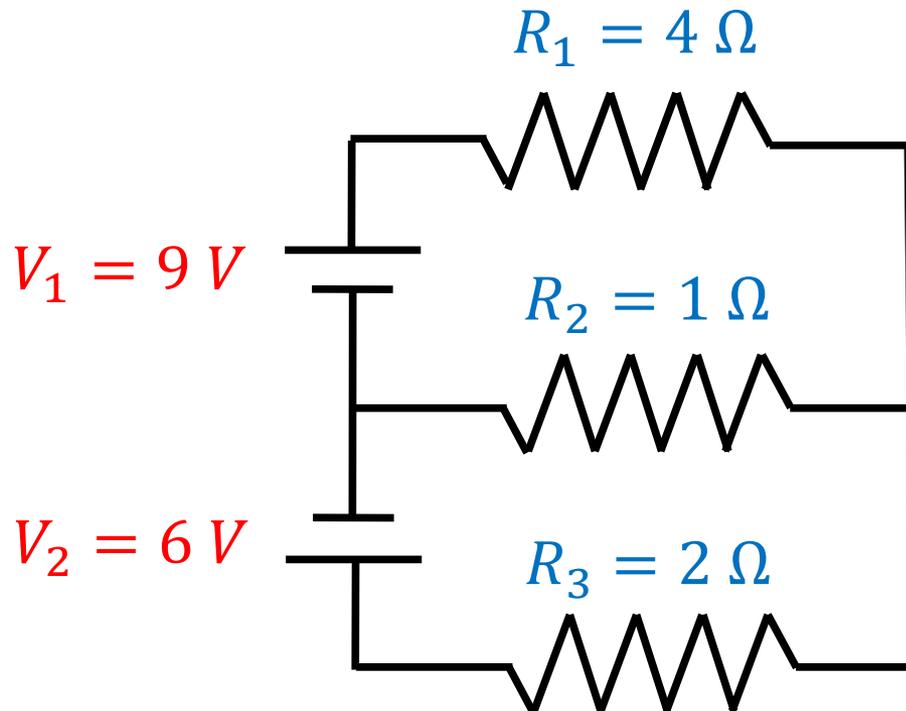
# Kirchoff's rules

- Sometimes we might need to analyse more complicated circuits, for example ...




Q) What are the currents flowing in the 3 resistors?

- Kirchoff's rules give us a systematic method
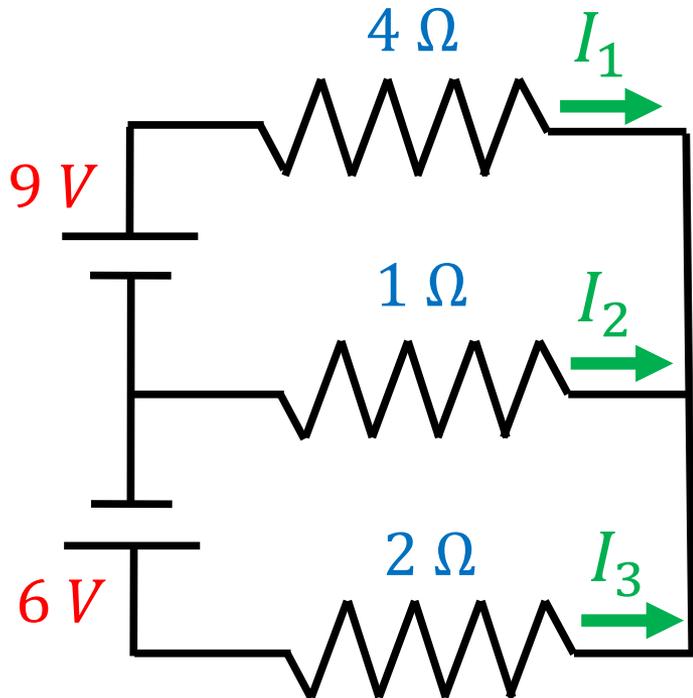
# Kirchoff's rules


- What are the currents flowing in the 3 resistors?



**Kirchoff's junction rule :**  
the sum of currents at  
any junction is zero
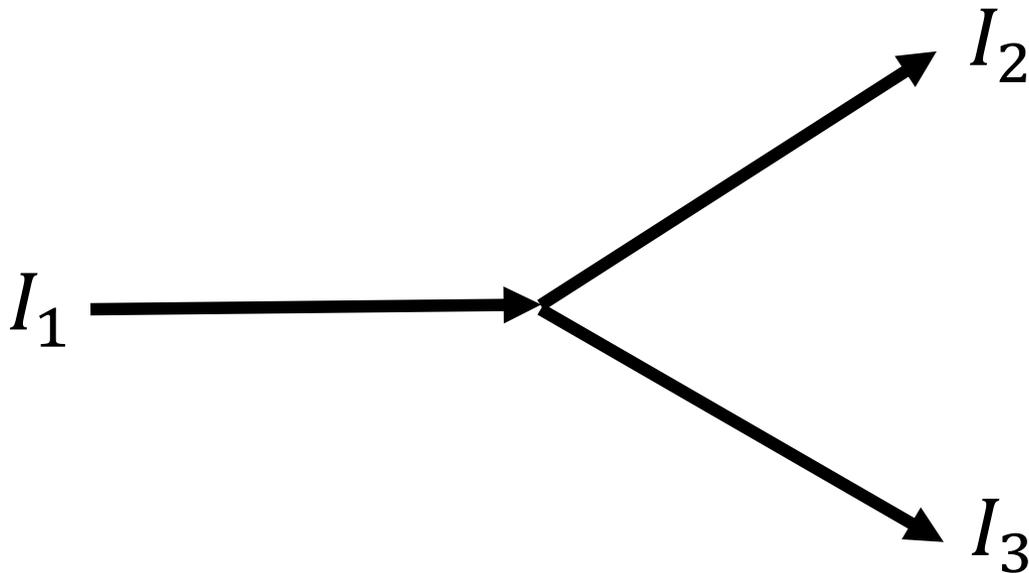
# Kirchoff's rules

- The sum of currents at any junction is zero
- Watch out for directions : into a junction is positive, out of a junction is negative




$$I_1 - I_2 - I_3 = 0$$


$$I_1 = I_2 + I_3$$
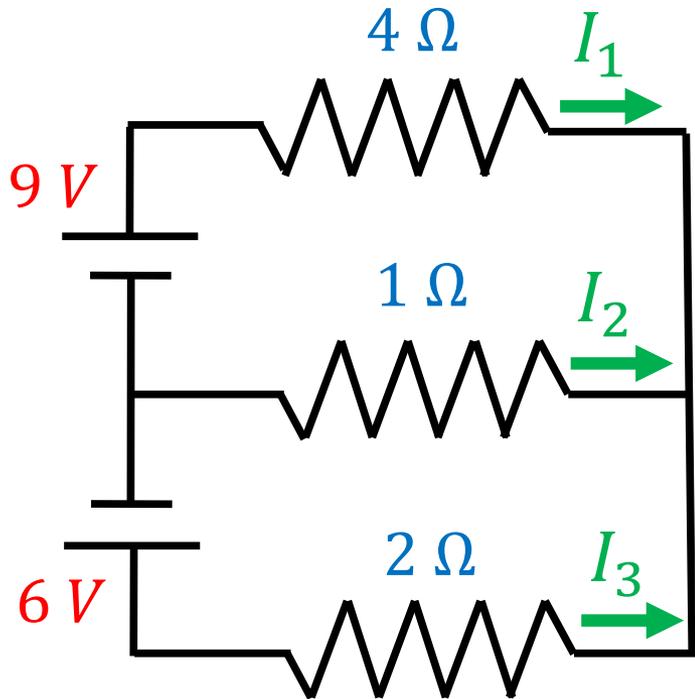
# Kirchoff's rules

- What are the currents flowing in the 3 resistors?



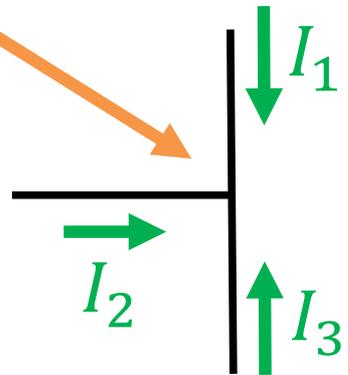
**Kirchoff's junction rule :**  
the sum of currents at  
any junction is zero




$$I_1 + I_2 + I_3 = 0$$
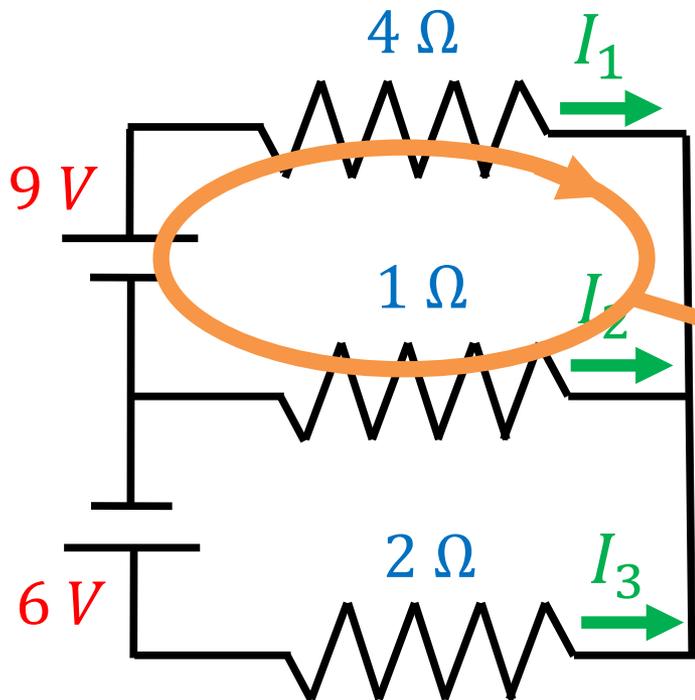
# Kirchoff's rules

- What are the currents flowing in the 3 resistors?




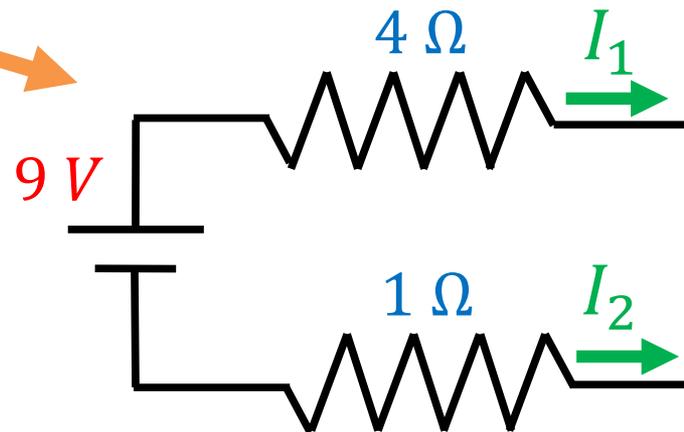**Kirchoff's loop rule** : the sum of voltage changes around a closed loop is zero


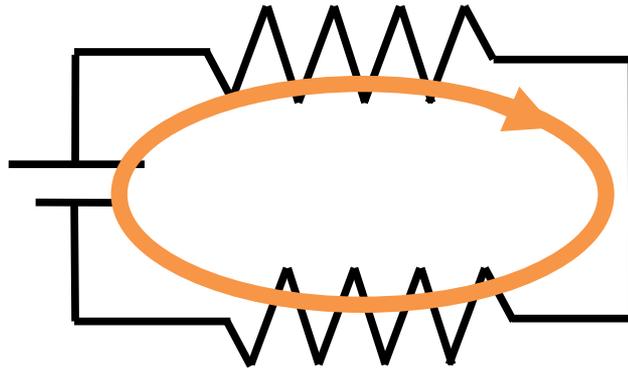
# Kirchoff's rules


- Sum of voltage changes around a closed loop is zero




- Consider a unit charge ( $Q=1$  Coulomb) going around this loop
- It gains energy from the battery (voltage change  $+V$ )
- It loses energy in the resistor (voltage change  $-I R$ )
- Conservation of energy :  $V - I R = 0$  (or as we know,  $V = I R$ )
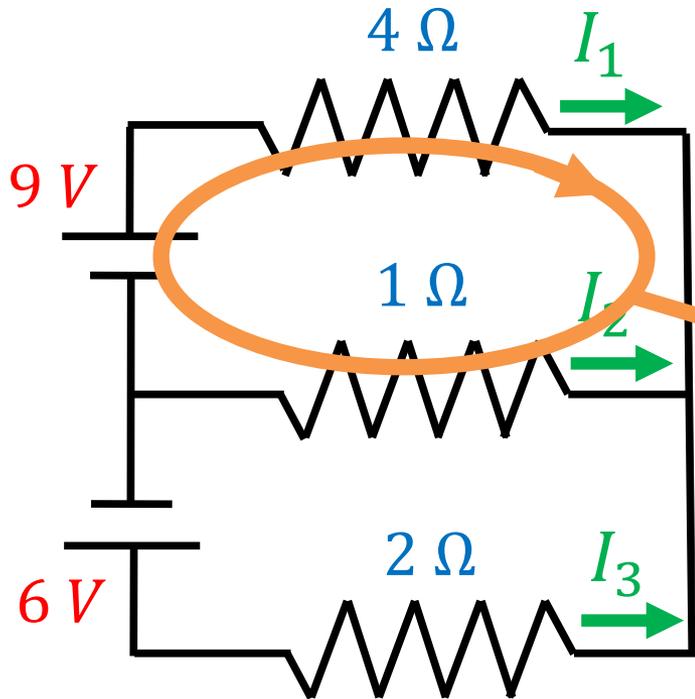
# Kirchoff's rules

- What are the currents flowing in the 3 resistors?



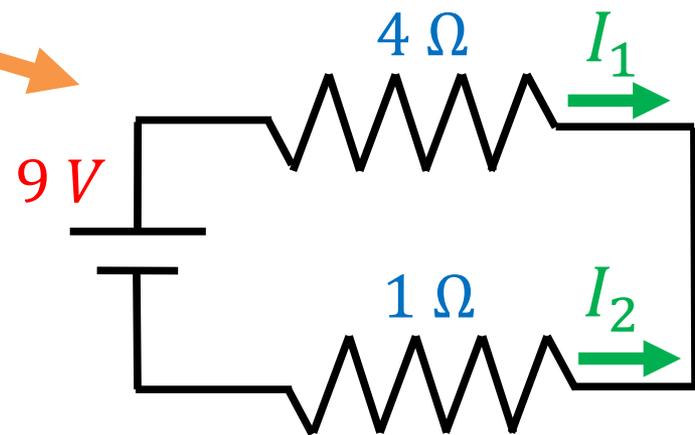
**Kirchoff's loop rule** : the sum of voltage changes around a closed loop is zero



$$9 - 4 I_1 + 1 I_2 = 0$$
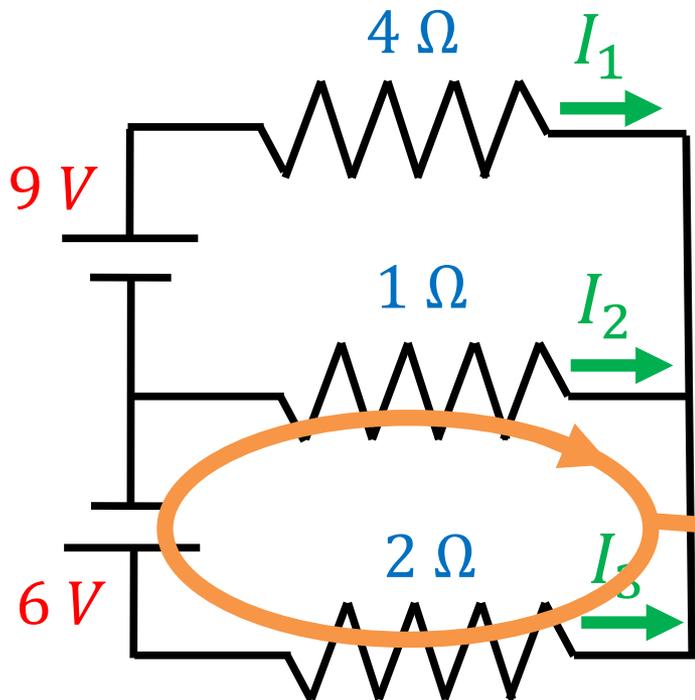
# Kirchoff's rules

- What are the currents flowing in the 3 resistors?




**Kirchoff's loop rule** : the sum of voltage changes around a closed loop is zero

$$-6 - 1 I_2 + 2 I_3 = 0$$
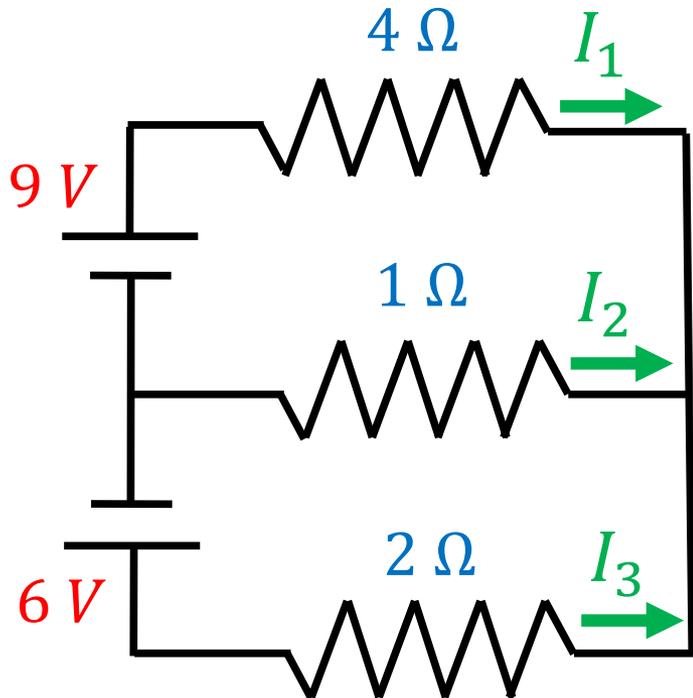
# Kirchoff's rules

- What are the currents flowing in the 3 resistors?



We now have 3 equations:

$$I_1 + I_2 + I_3 = 0 \quad (1)$$

$$9 - 4I_1 + I_2 = 0 \quad (2)$$

$$-6 - I_2 + 2I_3 = 0 \quad (3)$$


To solve for  $I_1$  we can use algebra to eliminate  $I_2$  and  $I_3$  :

$$(1) \rightarrow I_3 = -I_1 - I_2$$

$$\text{Sub. in (3)} \rightarrow I_2 = -2 - \frac{2}{3} I_1$$

$$\text{Sub. in (2)} \rightarrow I_1 = 1.5 \text{ A}$$

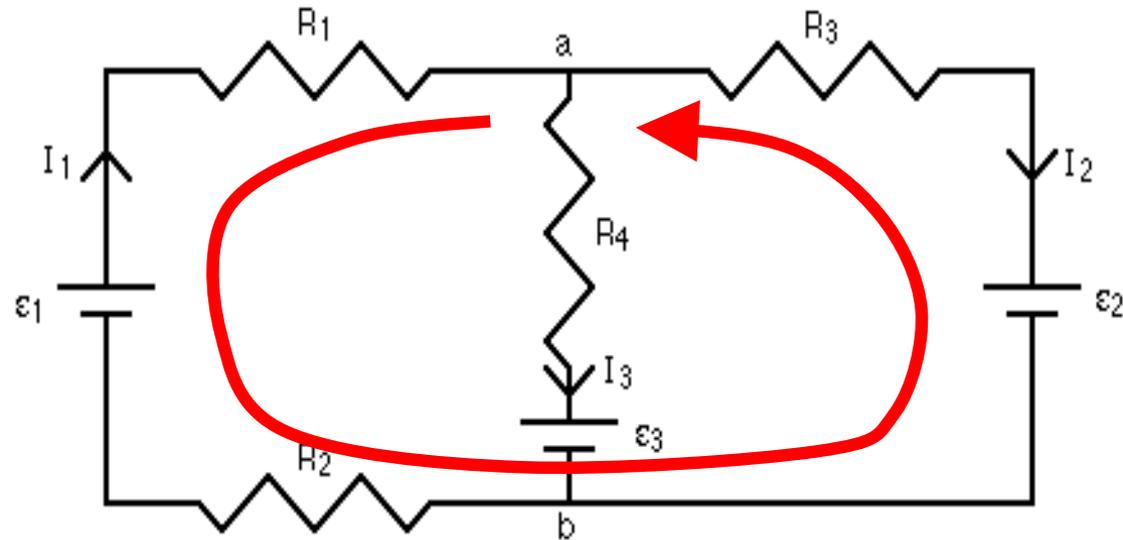Consider the loop shown in the circuit. The correct Kirchoff loop equation, starting at "a" is




$$1. \quad I_1 R_1 + \varepsilon_1 + I_1 R_2 + \varepsilon_2 + I_2 R_3 = 0$$

$$2. \quad -I_1 R_1 - \varepsilon_1 - I_1 R_2 - \varepsilon_3 - I_3 R_4 = 0$$

$$3. \quad I_1 R_1 - \varepsilon_1 + I_1 R_2 - \varepsilon_2 - I_2 R_3 = 0$$
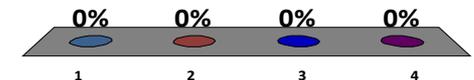
$$4. \quad I_1 R_1 - \varepsilon_1 + I_1 R_2 + \varepsilon_2 + I_2 R_3 = 0$$



# Chapter 25 summary

- Components in a **series** circuit all carry the **same current**
- Components in a **parallel** circuit all experience the **same potential difference**
- **Capacitors** are parallel plates which store equal & opposite charge  $Q = C V$
- **Kirchoff's junction rule** and **loop rule** provide a systematic method for analysing circuits